
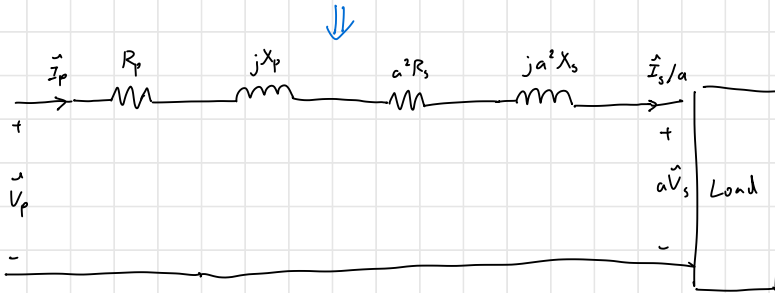


Example 9-1

A single-phase transformer has the following specifications:

20 kVA, 2400/240V, 60 Hz, full load at power factor of 0.8 lagging, $R_p = 0.8 \Omega$, $X_p = 3 \Omega$, $R_s = 0.008 \Omega$, and $X_s = 0.03 \Omega$.

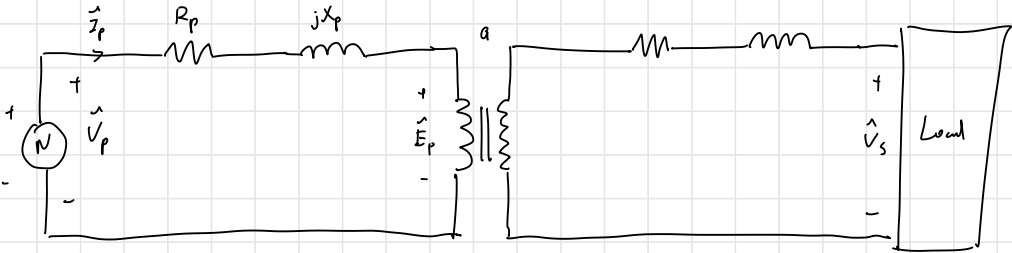- (a) Find the equivalent circuit parameters referred to primary. Draw the equivalent circuit diagram and phasor diagram referred to primary.
 (b) Find \vec{V}_p .



a. $a = \frac{N_p}{N_s} = \frac{2400}{240} = 10$, 20 kVA = maximum load that can be connected to secondary

$$R_{ep} = R_p + a^2 R_s = 0.8 + (10)^2 (0.008) = 1.6 \Omega$$


$$X_{ep} = X_p + a^2 X_s = 3 + (10)^2 (0.03) = 6 \Omega$$

2400/240

↑ ↑

$aV_s \neq V_p$ V_s

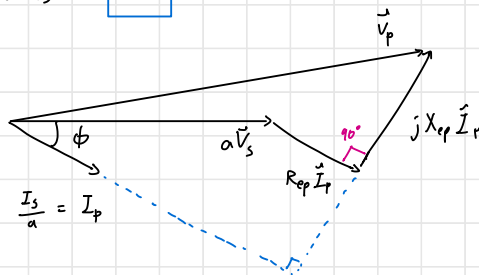$\frac{E_p}{E_s} = a$, $\frac{V_p}{V_s} \neq a$ ← not ideal



- $\vec{R}_{ep} \vec{I}_p$ is parallel to \vec{I}_p
- $jX_{ep} \vec{I}_p$ is perpendicular to \vec{I}_p (inductance)

$$b. \vec{V}_p = (R_{rp} + jX_{rp}) \vec{I}_r + a \vec{V}_s$$

$$\vec{V}_s = 240 \angle 0^\circ \text{ V}$$

$$a \vec{V}_s = 10 \vec{V}_s = 2400 \angle 0^\circ \text{ V}$$

$$\vec{I}_s = ?$$

$$|S| = V_s I_s \rightarrow I_s = \frac{|S|}{V_s} = \frac{20\,000}{240} = 83.3 \text{ A}$$

$$\phi = \cos^{-1} 0.8 = \angle -36.87^\circ \text{ A} \quad (\text{negative because lagging})$$

$$\therefore \hat{I}_s = 83.3 \text{ A} \angle -36.87^\circ \text{ A}$$

$$\hat{I}_r = \frac{I_s}{a} = 8.33 \angle -36.87^\circ \text{ A}$$

$$\vec{V}_p = (1.6 + j6)(8.33 \angle -36.87^\circ) + 2400 \angle 0^\circ$$

$$= 2440.86 \angle 0.75^\circ \text{ V}$$